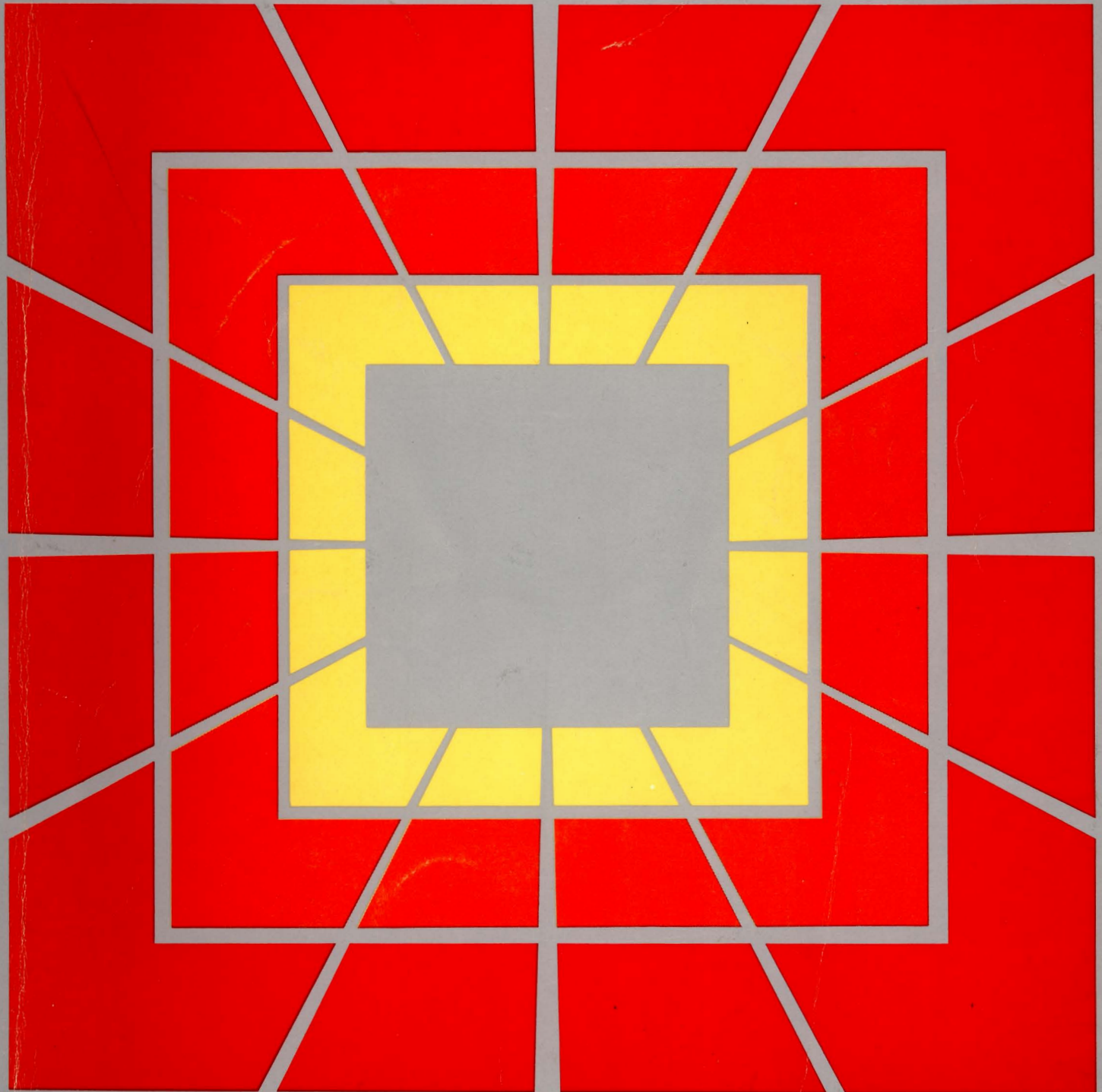


Electronics 5

DESIGNER'S CASEBOOK NUMBER



DESIGNERS CASEBOOK

Number 5

PREPARED BY THE EDITORS OF
Electronics

Fifth in a continuing series of selected Designer's Casebook sections of Electronics magazine. This edition includes Electronics issues from June 19, 1980 through November 3, 1981. Also included are feature articles and items from Engineer's Notebook of particular interest to the circuit designer.

CONTENTS

AUDIO AND ANALOG

- 2 Pulse modulator provides switched-mode amplification
- 3 Antilog amplifiers improve biomedical signal's S/N ratio
- 4 Bilateral speaker networks form switchless intercom
- 5 TTL line drivers link fiber optics
- 6 Dc-coupled trigger updates quickly
- 7 Optical age minimizes video measurement errors
- 8 Differential amp cancels integrator's crosstalk
- 9 On-chip transistors extend audio amp's design flexibility
- 12 On-chip transistors add versatility to op amp
- 14 Integrator improves 555 pulse-width modulator
- 15 Bi-FET op amps simplify AGC threshold design
- 16 Feedback reduces offset in wideband video amplifiers
- 17 Dual-function amp chip simplifies many circuits
- 20 Dual-function amplifier eases circuit design
- 23 Fm receiver mixes high gain with low power
- 24 Agc prevents noise build-up in voice-operated mike
- 25 Power-sharing bridge circuit improves amplifier efficiency
- 26 Bi-FET op amps invade 741's general-purpose domain
- 28 Current-biased transducer linearizes its response
- 29 Counter indicates when its probe is compensated
- 30 Transistor probe simplifies solid-state gaussmeter
- 32 Five-chip meter measures impedances ratiometrically
- 34 Charge-balancing modulator aids analog-signal isolation

CONTROL

- 36 Thermocouple simplifies temperature controller
- 37 Lamp dimmer fades in equidistant steps
- 38 Zero-crossing controller heats beakers noiselessly
- 39 One-chip tachometer simplifies motor controller
- 40 On/off timer maintains precision over wide range
- 41 Voltage-controlled resistance switches over preset limits
- 42 Divider sets tuning limits of C-MOS oscillator
- 43 Multiplier increases resolution of standard shaft encoders
- 44 Simplified multiplier improves standard shaft encoder
- 45 Fewer parts resolve shaft encoder data
- 46 Train speed controller ignores track resistance
- 47 Power-up relays prevent meter from pinning
- 48 Opto-isolated line monitor provides fail-safe control
- 50 Stepper resolves motor's angular position to 0.1°
- 51 Serial-data interface eases remote use of terminal keyboard
- 52 One-chip alarm scares auto thieves
- 53 Dual tones advance slides automatically
- 54 Current mirror linearizes remote-controlled timer
- 55 Low-cost controller stabilizes heater-type cryostats
- 56 Noise-immunized annunciator sounds change-of-state alarm
- 58 MOS FETs sequence power to sensitive op amps
- 59 Audio-visual controller synchronizes museum display

DESIGN

- 62 Two-chip radio link pilots toys and models
- 67 Transformerless inverter cuts photovoltaic system losses
- 73 Achieving stability in IC oscillators
- 80 Isolator stretches the bandwidth of two-transformer designs

FILTERS

- 89 Tracking filters demodulate two audio-band fm signals
- 90 Voltage controlled integrator sets filter's bandwidth
- 91 Inverting amplifier flips filter's response curve
- 92 Logic gate filter handles digital signals
- 94 Low-pass Chebyshev filters use standard-value capacitors
- 96 High-pass Chebyshev filters use standard-value capacitors

LOGIC

- 99 Dynamic logic probe displays five states
- 101 Digital comparator saves demultiplexing hardware
- 102 Digital comparator minimizes serial decoding circuitry
- 103 Dual one-shot keeps firmware on track
- 104 Index separator extracts all disk formats
- 105 Dual-feedback amplifier zeroes comparator hysteresis
- 107 Decoder logs signals' order of arrival
- 108 Four-chip meter measures capacitance to within 1%
- 109 Time-slot assigner chip cuts multiplexer parts count
- 110 Enhanced multiplexer cuts parts count
- 112 Pulse-width monitor flags poor timing
- 113 Improving the LM395 for low-level switching
- 114 Contact tester quantifies open-, short-circuit tendencies
- 115 PLL performs accurate phase measurements
- 116 Interfacing TTL with fast bipolar drivers
- 118 Adapter equips HP analyzer for general ROM tracing
- 119 LED indicates timing error in emitter-coupled logic one-shot
- 120 Wired-OR ECL one-shot has near-zero propagation time
- 121 Twin optocouplers raise serial transmission speed
- 122 Digital phase meter updates measurement each cycle

POWER SUPPLIES

- 125 One-chip voltage splitter conserves battery power
- 126 V-MOS oscillator ups converter's switching frequency
- 127 Low-loss shunt protects high-current supplies
- 128 Low-cost timers govern switched-mode regulator
- 129 Low-power inverter ignites gas-discharge lamps
- 130 Reed-coil relay is behind flexible fault detection
- 131 Milliampere current source is voltage-controlled
- 132 Power-fail detector uses chip's standby mode
- 134 High-current voltage regulator works with negative supplies
- 135 Regulator boosts supply voltage for programming EE-PROMs
- 137 Stacked voltage references improve supply's regulation
- 138 Comparator circuit regulates battery's charging current

SIGNAL CONVERSION

- 140 One-chip DVM displays two-input logarithmic ratio
- 141 Serial-to-parallel converter decodes width-modulated BCD
- 142 Switched V-f converter linearizes analog multiplier
- 143 Voltage-detector chip simplifies V-f converter
- 144 Low-power f-v converter turns portable tachometer
- 145 Integrator improves 555 pulse-width modulator

-
- 146 Dithering display expands bar graph's resolution
 - 148 Multiplexers compress data for logarithmic conversion
 - 150 Low-cost coordinate converter rotates vectors easily
 - 152 Adapting a home computer for data acquisition

SIGNAL SOURCES

- 155 FSK transmitter uses two gated oscillators
- 156 Simple sound generator takes orders from microcomputer
- 158 Op-amp summer forms simple high-speed phase generator
- 160 Adjustable e^x generator colors synthesizer's sounds
- 161 Two-chip generator shapes synthesizer's sounds
- 162 Sync clock, counter improve programmable-width generator
- 163 Four chips generate pseudorandom test data
- 164 Two-chip pulse generator operates at 75 MHz
- 165 Deglitcher-delay circuit serves also as pulse generator
- 166 Low-cost generator delivers all standard bit rates